

172.16.5.43 address in the dialog box.  
Folder needs to be copied to the \\172.16.5.43\Exam Submission 2024\Afnan\BCS-2A.

Student Name \_\_\_\_\_

Roll No \_\_\_\_\_

Section \_\_\_\_\_

Student Signature \_\_\_\_\_

**CLO # 1: Identify and explain fundamental concepts of digital logic design including basic and universal gates, number systems, binary coded system, basic components of combinational and sequence circuits.**

**Q1. [= 10 marks]**

Alice and Bob are competing in a mathematics quiz where each participant's score is represented by a 2-bit binary number. They want to know who has the higher score without revealing their exact scores to each other. Design a circuit that takes Alice's and Bob's scores as inputs and outputs a signal indicating who has the higher score, or if they are tied. **Show complete working.**

**CLO # 2: Demonstrate the acquired knowledge to apply techniques related to the design and analysis of digital electronics circuits, including Boolean Algebra and Multi-variable Karnaugh map methods.**

**Q2. [15 = 7.5+7.5 marks]**

- a) Design a 3x2 Multiplier by first deriving the complete equation for the circuit. Show the output on a 7-Segment display, use the first 4 outputs for one display while the remaining output should be connected to in such a way that final output shows 88.

## National University of Computer and Emerging Sciences

- b) Complete the truth table below for a Boolean Function which is defined to be true, output in the table is 1, when all or at least two of input variables are 0. Complete the truth-table and draw a Karnaugh map for the output F. The Boolean expression should be a (sum of products) expression, but implement the circuit using all NAND-NAND Logic gates. Draw a diagram of your circuit.

A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

---

**CLO # 3: Analyze small-scale combinational digital circuits.**

---

**Q3: [7.5+7.5 =marks]**

---

u're a robotics engineer...

0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

---

**CLO # 3: Analyze small –scale combinational digital circuits.**

---

**Q3: [7.5+7.5 =marks]**

- You're a robotics engineer working on a modular robot system. The robot can be configured with three different modules (Module A, Module B, and Module C), each with two operational modes (Mode X and Mode Y). Your task is to design a logic circuit on Logic works that efficiently displays the chosen configuration using LEDs, allowing users to see which modules are active and in which mode they are operating.
- Using the BCD to Seven Segment Decoder implement a circuit that displays the **LAST four** Digits of your roll number, the implementation should also eliminate trailing zeros. **(The digits should be on screen when the file is opened else no marks will be given)**

---

**CLO # 4: Design small-scale combinational and synchronous sequential digital circuit using Boolean Algebra and K-map.**

---

**Q4: [5+5= 10 marks]**

- Implement JK flip-flop using ICs on logic works also make truthtable.

**Note:** You have to show the circuit diagram.

that efficiently displays the chosen configuration using LEDs, allowing users to see which modules are active and in which mode they are operating.

- b) Using the BCD to Seven Segment Decoder implement a circuit that displays the **LAST four** Digits of your roll number, the implementation should also eliminate trailing zeros. **(The digits should be on screen when the file is opened else no marks will be given)**

---

**O # 4: Design small-scale combinational and synchronous sequential digital circuit using Boolean algebra and K-map.**

---

: [5+5= 10 marks]

- a) Implement JK flip-flop using ICs on logic works also make truthtable.  
**Note:** You have to Show the set, reset and toggle states through timing diagram attach the screenshots for the timing diagram in the Word file with comments to explain each output.
- b) Design 16 by 1 multiplexer circuit on Logic works by using 4 by 1 multiplexer.